
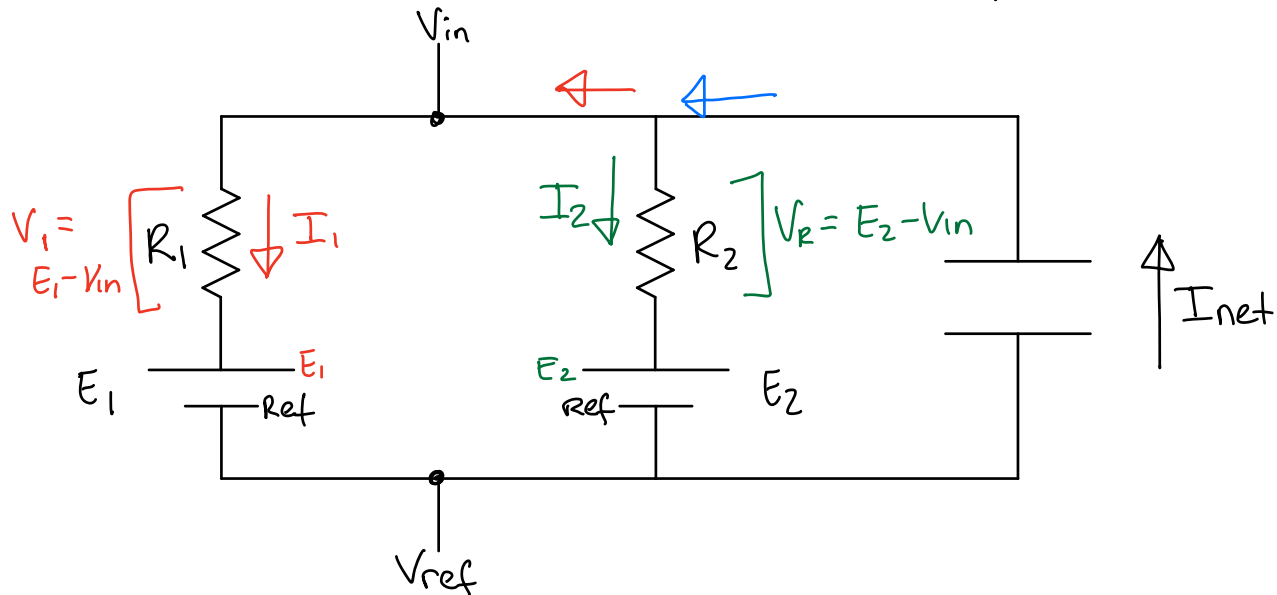


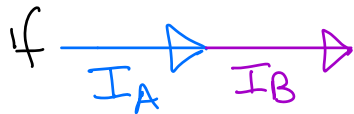* Arrow directions are "arbitrary" (don't matter initially) BUT must then be self-consistent across equations




* Arrow direction for the current determines the *sign* of the current

$$I_{net} = +I_1 + I_2$$




then $+I_A = +I_B$

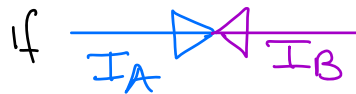

then $+I_A = -I_B$

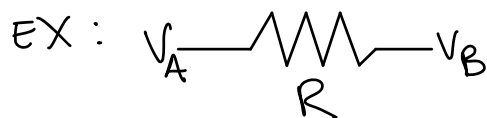* Sign (direction) of the current depends on the directionality of voltage (in this case across the resistor)



then, $V_B > V_A$



then, $V_B < V_A$

So, if $I_{net} = +I_1 + I_2$ then $V_{R1} = E_1 - V_{in}$
and $V_{R2} = E_2 - V_{in}$


and these equations combine to:

$$0 = +\frac{E_1 - V_{in}}{R_1} + \frac{E_2 - V_{in}}{R_2}$$

(simplifies) \Downarrow

$$V_{in} = \frac{[E_1/R_1 + E_2/R_2]}{(1/R_1 + 1/R_2)}$$

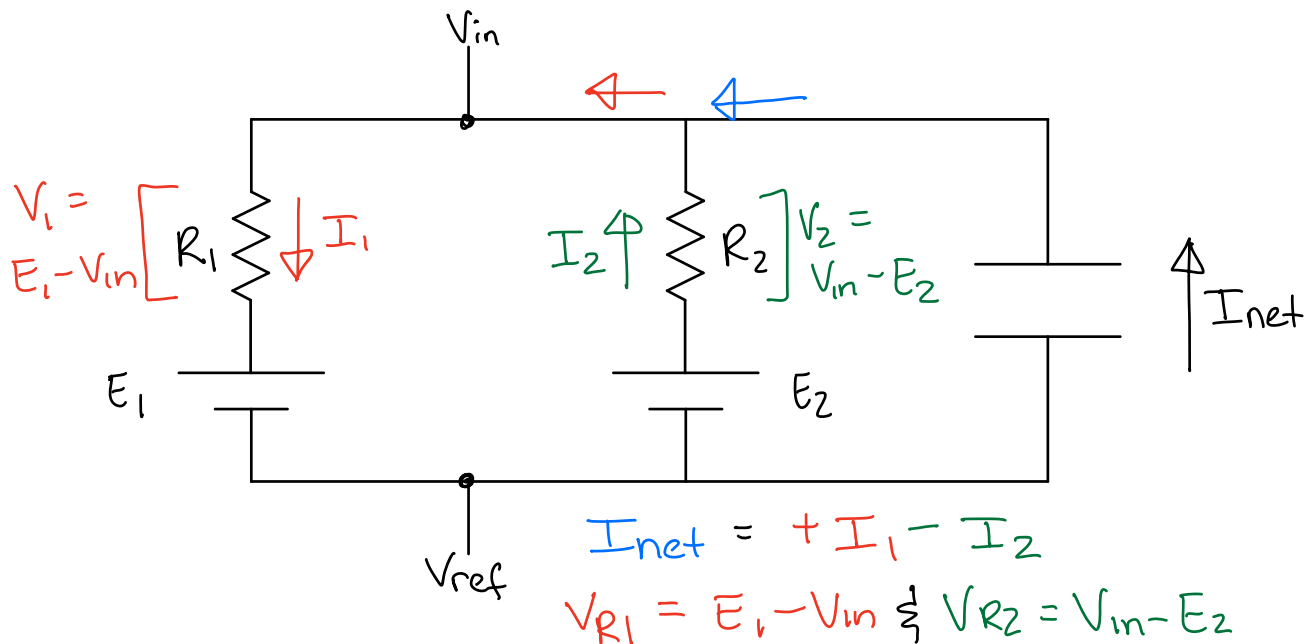* If you choose different arrow directions, all other equation "signs" must stay consistent with that arrow choice. *



$$0 = +\frac{E_1 - V_{in}}{R_1} - \frac{V_{in} - E_2}{R_2}$$

\Downarrow * (simplifying steps)

$$V_{in} = \frac{[E_1/R_1 + E_2/R_2]}{(1/R_1 + 1/R_2)}$$

$$* \begin{cases} 0 = +\frac{E_1}{R_1} - \frac{V_{in}}{R_1} - \frac{V_{in}}{R_2} + \frac{E_2}{R_2} \\ V_{in} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{E_1}{R_1} + \frac{E_2}{R_2} \end{cases}$$